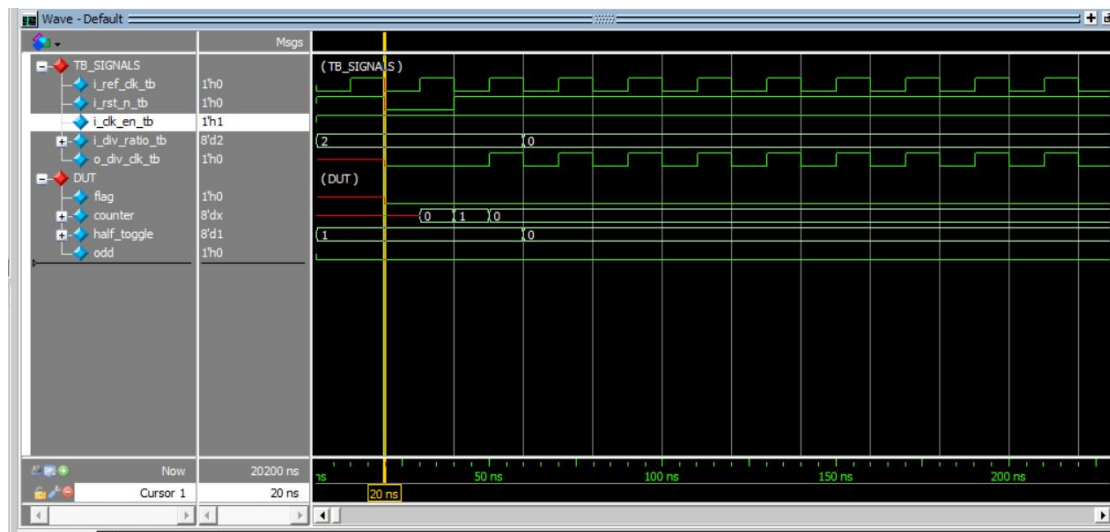


CLOCK_DIVIDER


1. test case 1 : test reset:

O_div_clk=0




2. test case 2 : test o_div_clk=i_ref_clk

1. I_div_ratio=0:

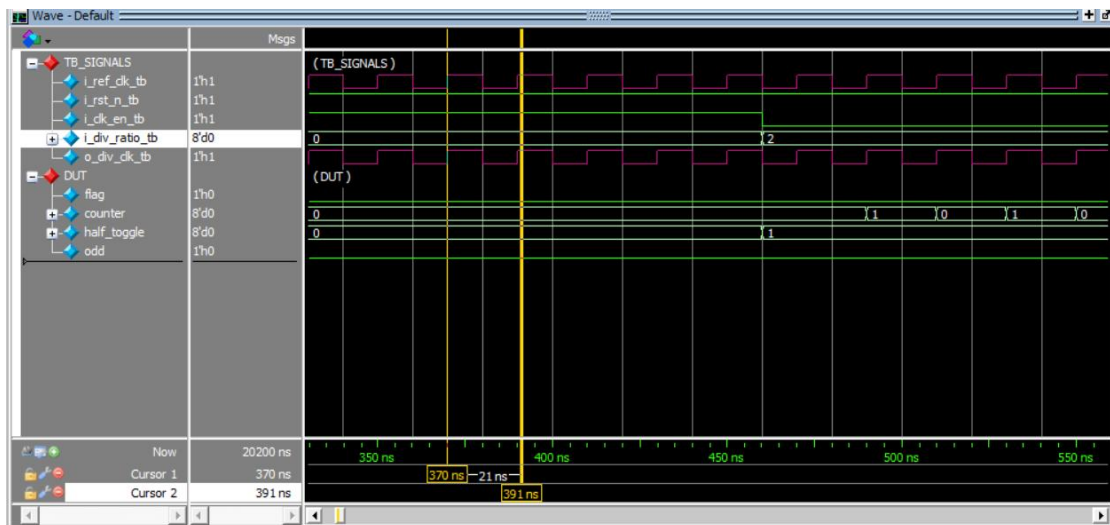


2. I_div_ratio=2, I_clk_en=0:

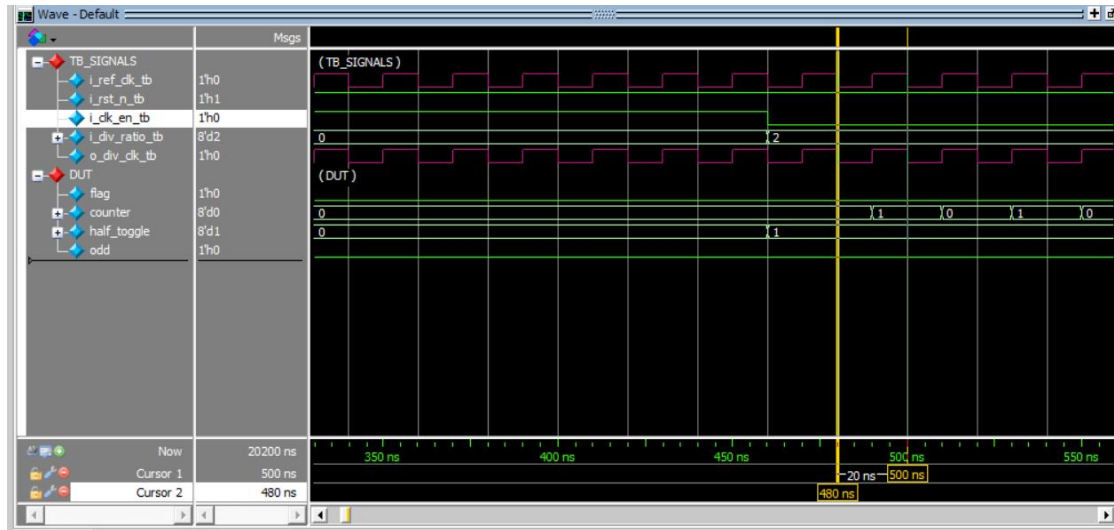


3. test case 3 : test even I_div_ratio:


1. I_div_ratio=2:

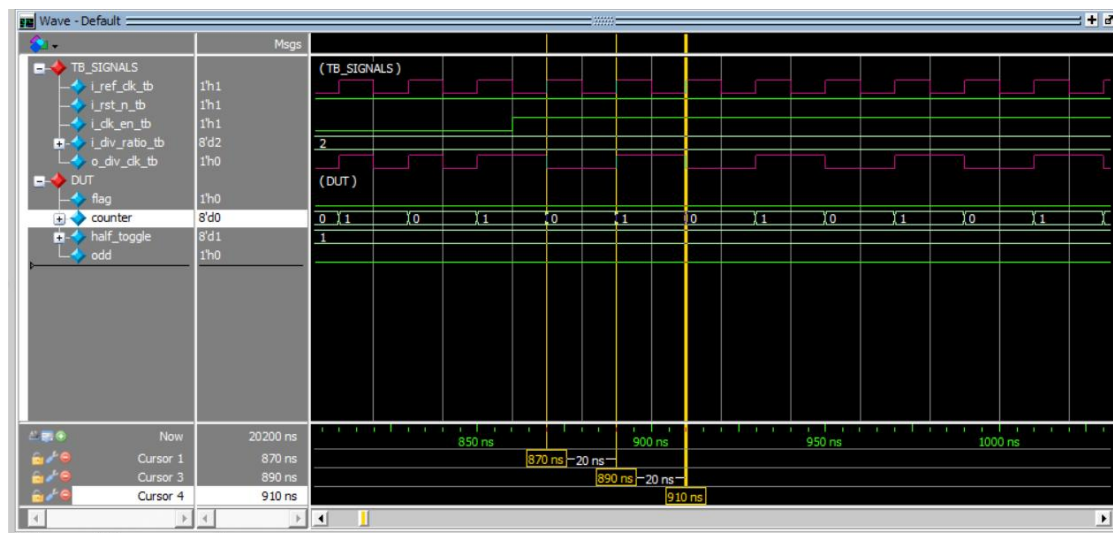


2. I_div_ratio=4:

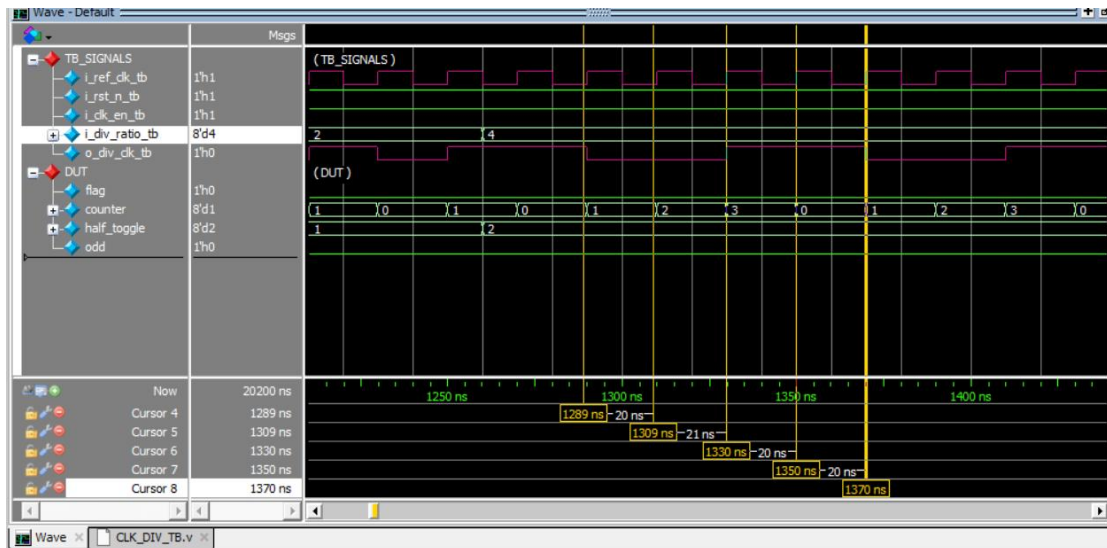


3. I_div_ratio=8:

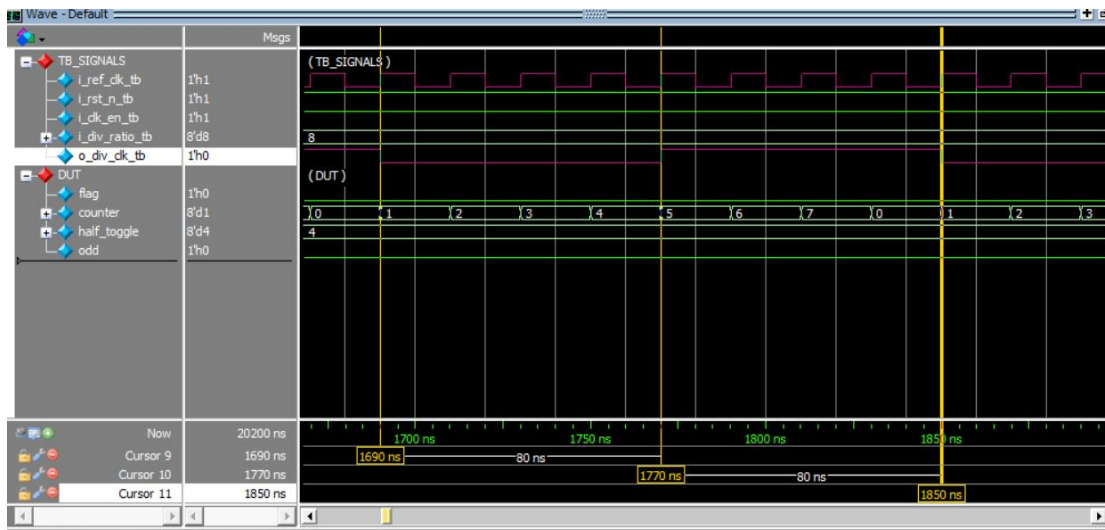

4. I_div_ratio=16:

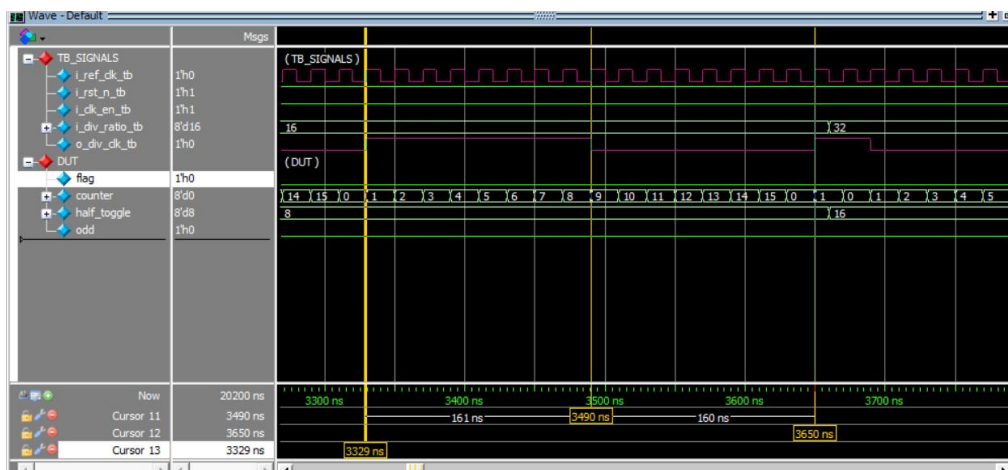


5.l_div_ratio=32:

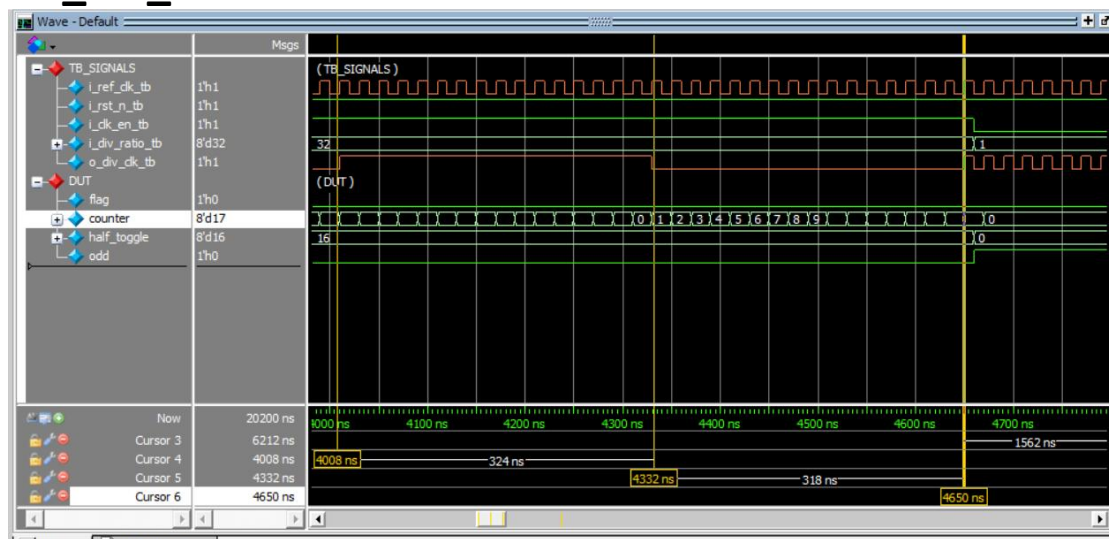


4. test case 4 : test odd div_ratio:


1.l_div_ratio=1:

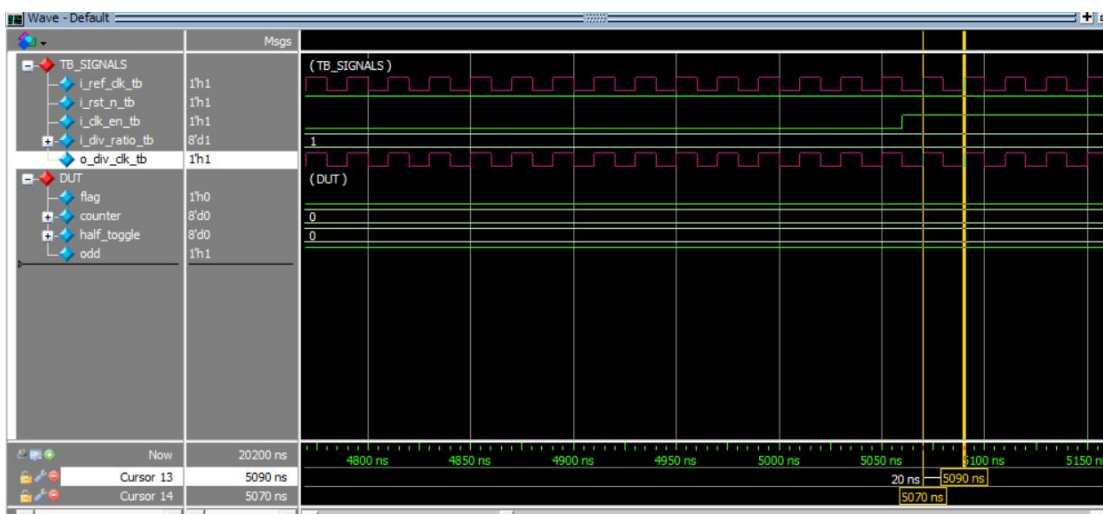


2.1_div_ratio=3:

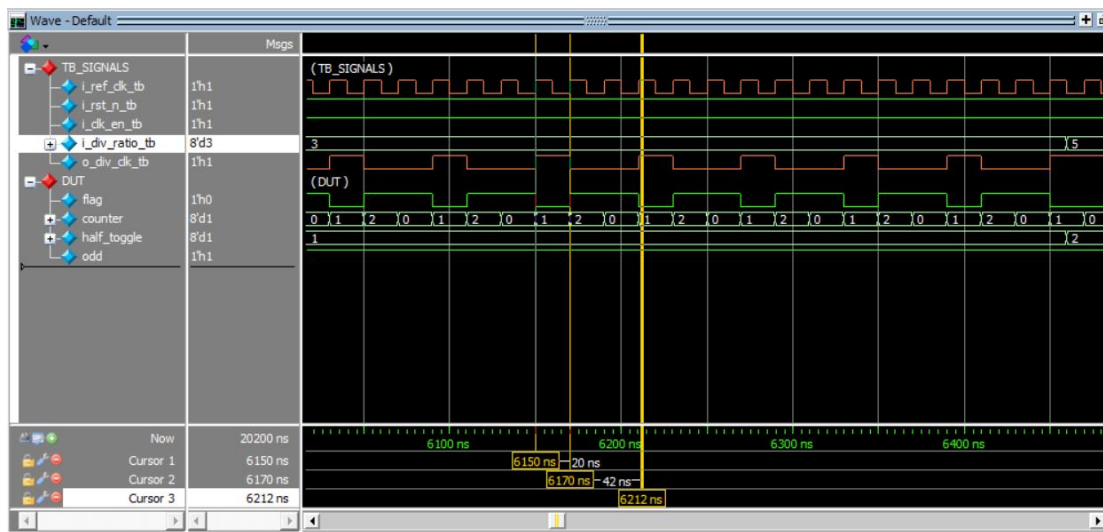


3. $i_div_ratio=5$:

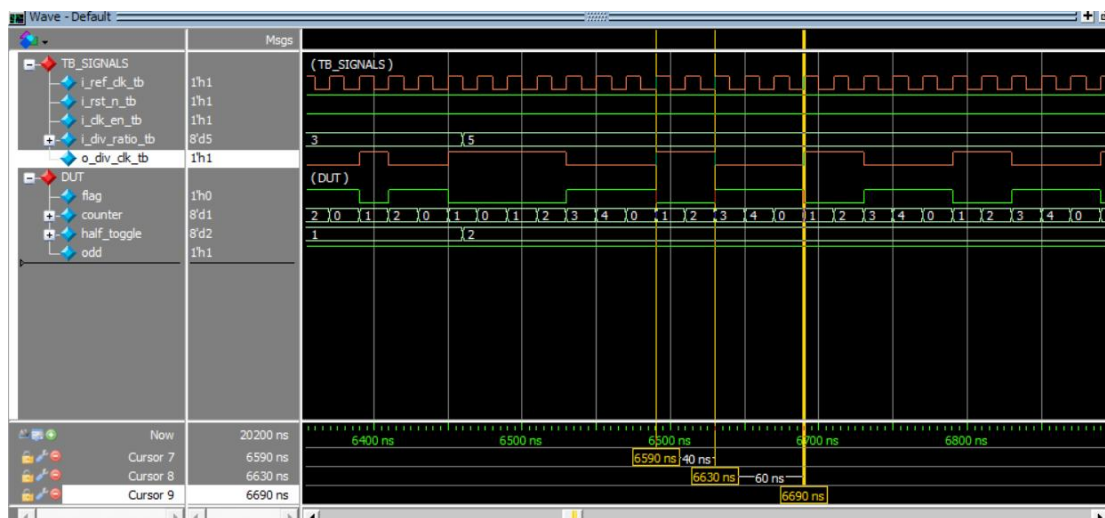


4. $i_div_ratio=7$:

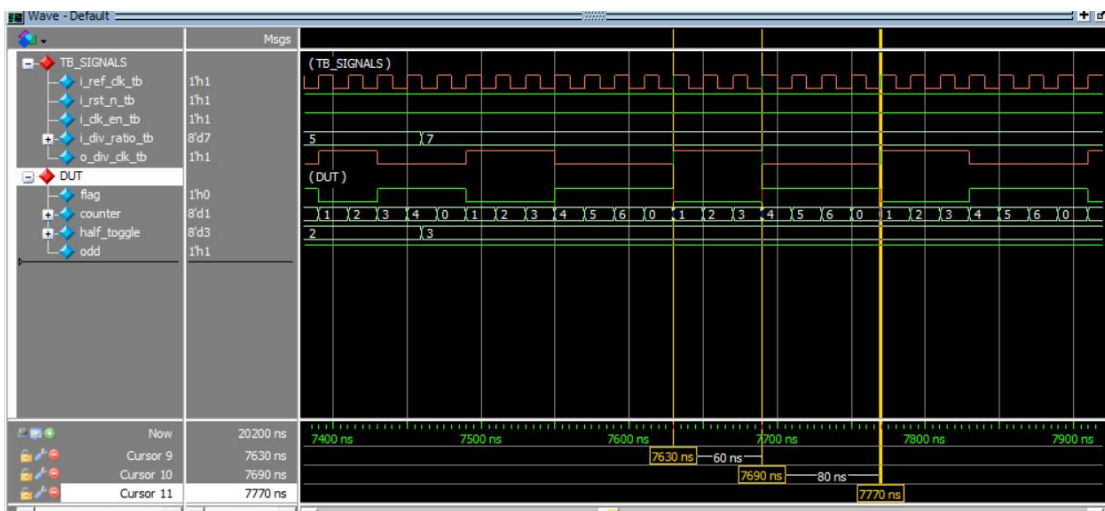


5. $i_div_ratio=9$:

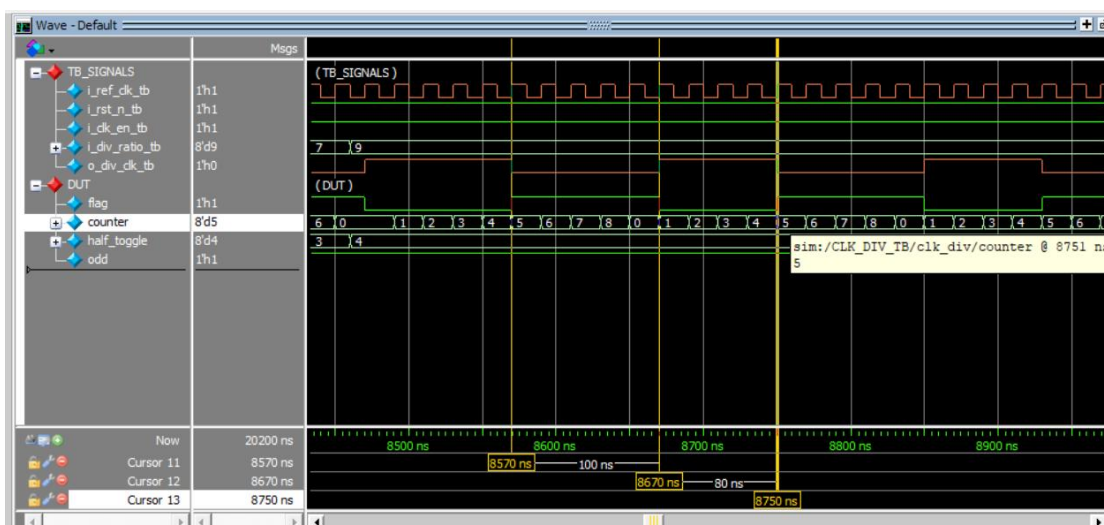


6. $i_div_ratio=11$:

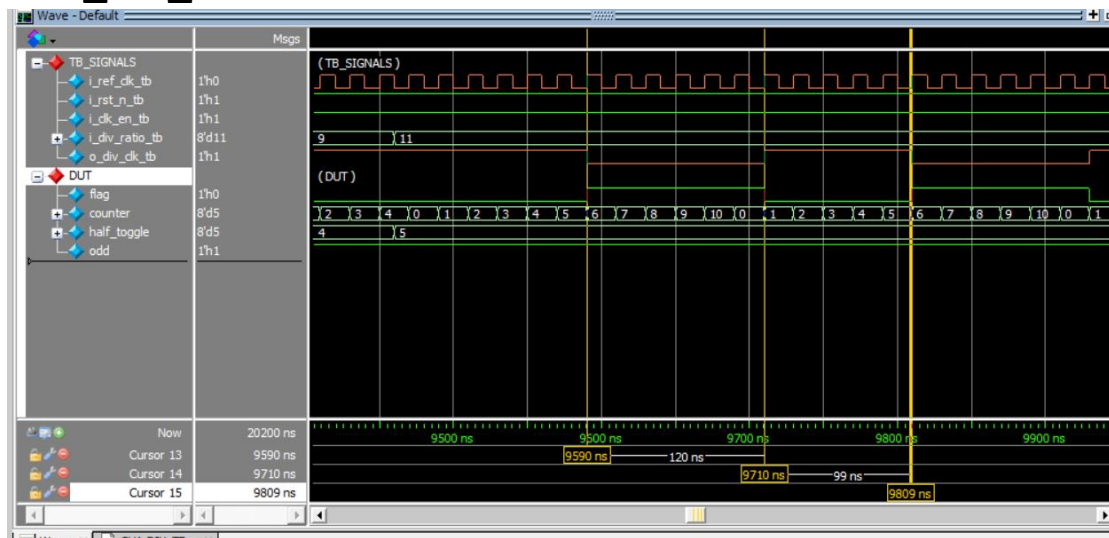


7. $i_div_ratio=13$:

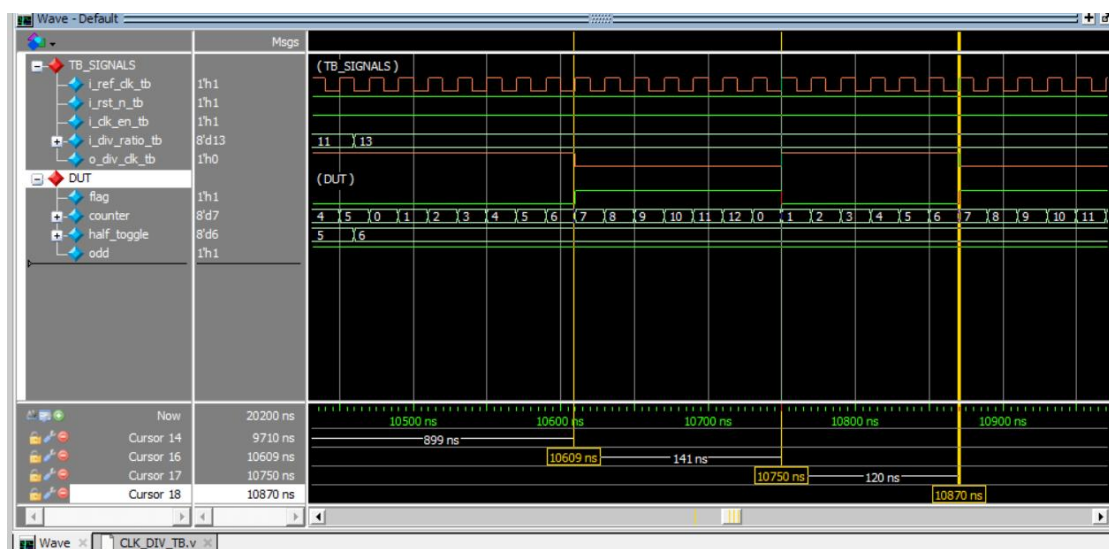


8. $i_div_ratio=15$:

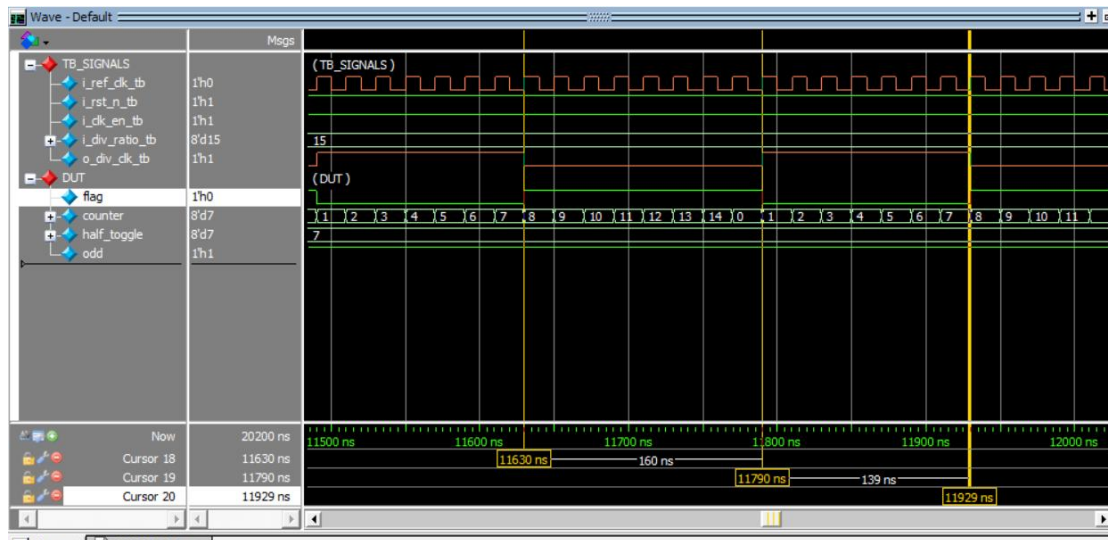

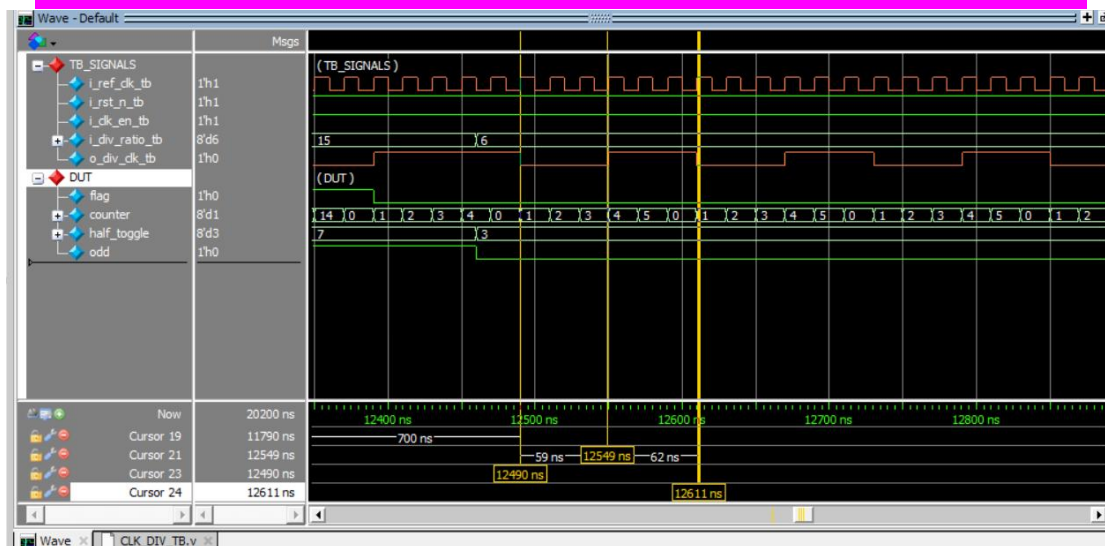5. test case 5 :transition from odd to even:



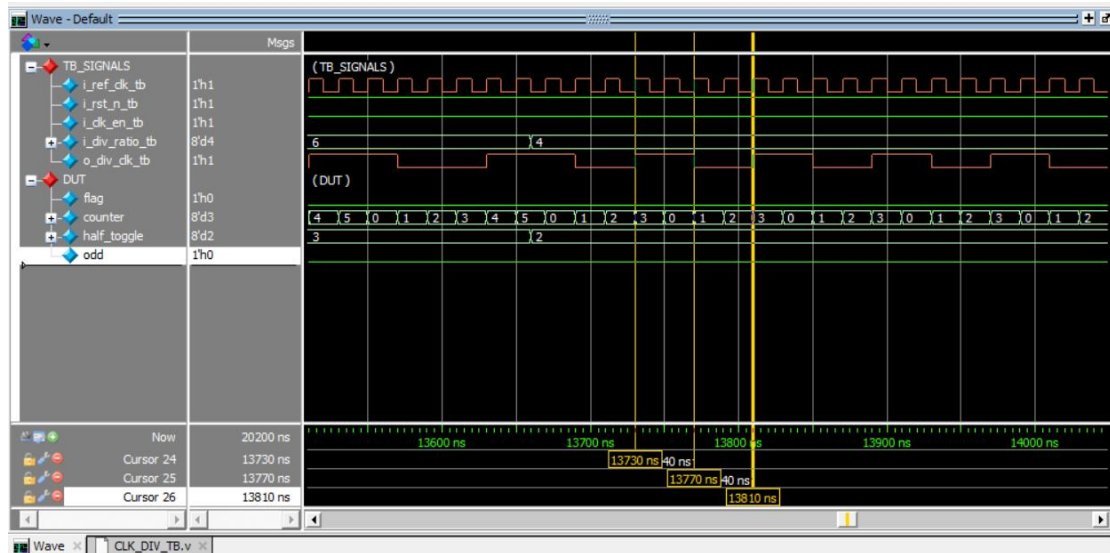6. test case 6 :transition from 6 to 4
div_ratio:



7. test case 7 : transition from 7 to 5:

